



1 DEFINITIONS

1. The unit step function is

$$u(t) = \begin{cases} 1 & t > 0 \\ \frac{1}{2} & t = 0 \\ 0 & t < 0 \end{cases} \quad (1.1)$$

2. The Laplace transform of $g(t)$ is defined as

$$G(s) = \int_{-\infty}^{\infty} g(t)e^{-st} dt \quad (1.2)$$

3. In the circuit, the switch S is connected to position P for a long time so that the charge on the capacitor becomes $q_1 \mu C$. Then S is switched to position Q . After a long time, the charge on the capacitor is $q_2 \mu C$.

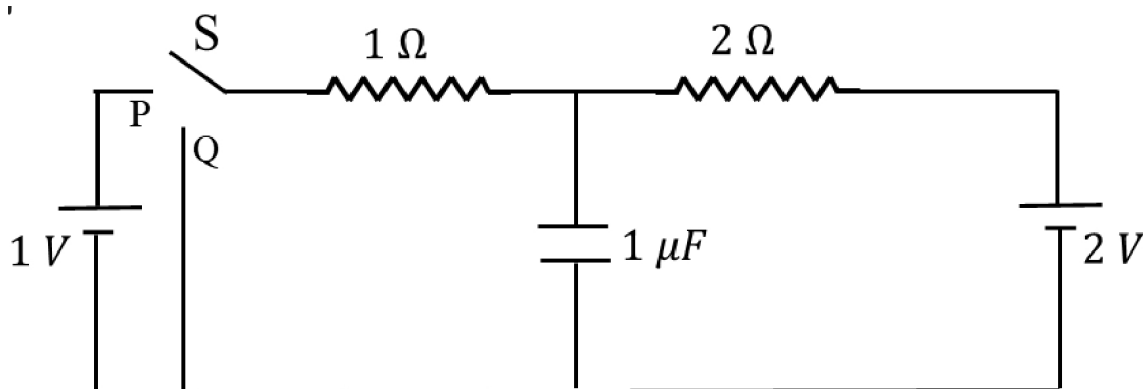


Fig. 1.1

2 PROBLEMS

- Find q_1 .
- Show that the Laplace transform of $u(t)$ is $\frac{1}{s}$ and find the ROC.
- Show that

$$e^{-at}u(t) \xleftrightarrow{\mathcal{L}} \frac{1}{s+a}, \quad a > 0 \quad (2.1)$$

and find the ROC.

4. Now consider the following resistive circuit transformed from Fig. 1.1 where

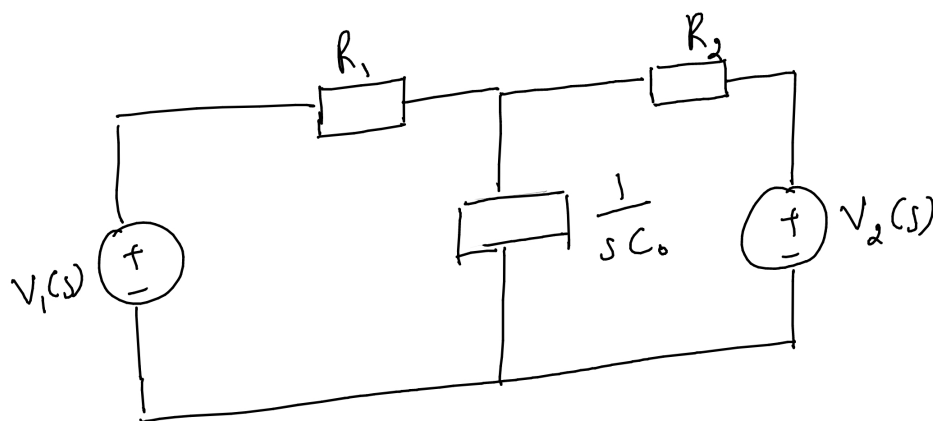


Fig. 2.1

$$u(t) \xleftrightarrow{\mathcal{L}} V_1(s) \quad (2.2)$$

$$2u(t) \xleftrightarrow{\mathcal{L}} V_2(s) \quad (2.3)$$

Find the voltage across the capacitor $V_{C_0}(s)$.

5. Find $v_{C_0}(t)$.