

# Circuits and Transforms

G V V Sharma\*

## CONTENTS

1	<b>Definitions</b>	1
2	<b>Laplace Transform</b>	1
3	<b>Initial Conditions</b>	1

*Abstract*—This manual provides a simple introduction to Transforms

## 1 DEFINITIONS

1. The unit step function is

$$u(t) = \begin{cases} 1 & t > 0 \\ \frac{1}{2} & t = 0 \\ 0 & t < 0 \end{cases} \quad (1.1)$$

2. The Laplace transform of  $g(t)$  is defined as

$$G(s) = \int_{-\infty}^{\infty} g(t)e^{-st} dt \quad (1.2)$$

## 2 LAPLACE TRANSFORM

1. In the circuit, the switch S is connected to position P for a long time so that the charge on the capacitor becomes  $q_1 \mu C$ . Then S is switched to position Q. After a long time, the charge on the capacitor is  $q_2 \mu C$ .

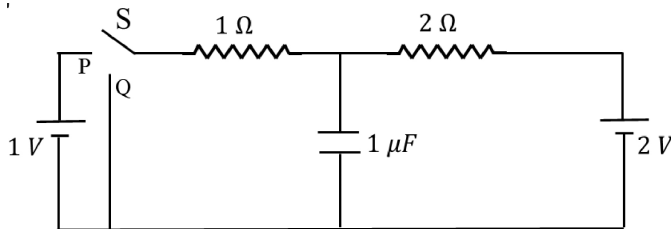


Fig. 2.1

\*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in the manuscript is released under GNU GPL. Free to use for anything.

2. Draw the circuit using latex-tikz.
3. Find  $q_1$ .
4. Show that the Laplace transform of  $u(t)$  is  $\frac{1}{s}$  and find the ROC.
5. Show that

$$e^{-at}u(t) \xleftrightarrow{\mathcal{H}} L \frac{1}{s+a}, \quad a > 0 \quad (2.1)$$

and find the ROC.

6. Now consider the following resistive circuit transformed from Fig. 2.1 where

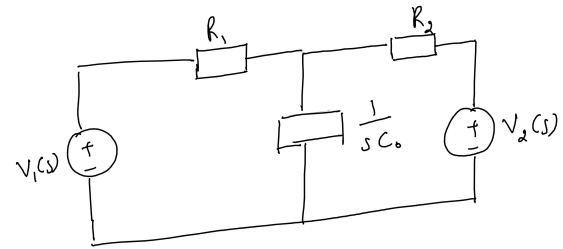


Fig. 2.2

$$u(t) \xleftrightarrow{\mathcal{H}} LV_1(s) \quad (2.2)$$

$$2u(t) \xleftrightarrow{\mathcal{H}} LV_2(s) \quad (2.3)$$

Find the voltage across the capacitor  $V_{C_0}(s)$ .

7. Find  $v_{C_0}(t)$ . Plot using python.
8. Verify your result using ngspice.
9. Obtain Fig. 2.2 using the equivalent differential equation.

## 3 INITIAL CONDITIONS

1. Find  $q_2$  in Fig. 2.1.
2. Draw the equivalent  $s$ -domain resistive circuit when S is switched to position Q. Use variables  $R_1, R_2, C_0$  for the passive elements. Use latex-tikz.
3.  $V_{C_0}(s) = ?$
4.  $v_{C_0}(t) = ?$  Plot using python.
5. Verify your result using ngspice.
6. Find  $v_{C_0}(0-), v_{C_0}(0+)$  and  $v_{C_0}(\infty)$ .

7. Obtain the Fig. in problem 3.2 using the equivalent differential equation.